

# Theory Assignment

Answer in no more than 6 pages total  
Minimum 10pt font size

August 4, 2014

1. **(Multiplier)** Consider the operational amplifier circuit in Figure 1. Draw an equivalent circuit using the model for an operational amplifier including input resistance  $R_i$ , output resistance  $R_o$  and open loop gain  $A$  (given in Figure 2.5 of the lecture notes). Analyse this circuit to obtain a relationship between the input voltage signal  $x$  and output voltage signal  $y$ . By taking limits as  $R_i \rightarrow \infty$ ,  $A \rightarrow \infty$  and  $R_o \rightarrow 0$  find an expression relating  $x$  and  $y$  assuming that the operational amplifier is ideal. Obtain the same expression directly using the rules for analysing ideal operational amplifiers. Is the system that describes this circuit stable? Is it regular?
2. **(Properties of signals)** Plot each of the following signals and show whether they are: bounded, periodic, absolutely integrable, square integrable.
  - (a)  $x(t) = 1$
  - (b)  $x(t) = u(t+1)e^{-t}$  where  $u(t)$  is the step function
  - (c)  $x(t) = \sin(2\pi t)\cos(\pi t)$
  - (d)  $x(t) = \frac{\sin^2(\pi t)}{\pi t}$

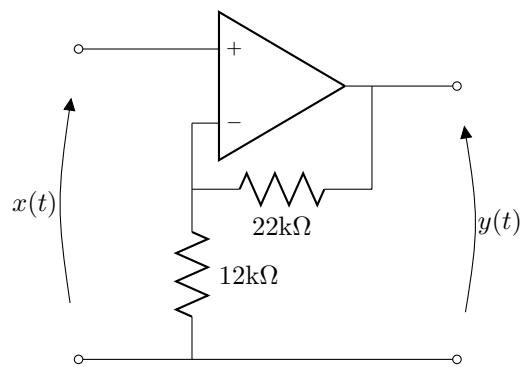


Figure 1: Operational amplifier circuit configured as a multiplier